

# Control Systems

G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Feedback Voltage Amplifier: Series-Shunt</b>	<b>1</b>
<b>2</b>	<b>Feedback Current Amplifier: Shunt-Series</b>	<b>1</b>
2.1	Ideal Case . . . . .	1
2.2	Practical Case . . . . .	1
<b>3</b>	<b>Feedback Current Amplifier: Example</b>	<b>1</b>
<b>4</b>	<b>Feedback Transconductance Amplifier: Series-Series</b>	<b>1</b>
<b>5</b>	<b>Feedback Problem</b>	<b>1</b>

**Abstract**—This manual is an introduction to control systems in feedback circuits. Links to sample Python codes are available in the text.

Download python codes using

svn co <https://github.com/gadepall/school/trunk/control/feedback/codes>

1 FEEDBACK VOLTAGE AMPLIFIER: SERIES-SHUNT

2 FEEDBACK CURRENT AMPLIFIER: SHUNT-SERIES

2.1 Ideal Case

2.2 Practical Case

3 FEEDBACK CURRENT AMPLIFIER: EXAMPLE

4 FEEDBACK TRANSCONDUCTANCE AMPLIFIER:  
SERIES-SERIES

5 FEEDBACK PROBLEM

5.1. A two-pole amplifier for which  $G_o = 10^3$  and having poles at 1 MHz and 10 MHz is to be connected as a differentiator. On the basis of the rate-of-closure rule, what is the smallest differentiator time constant for which operation

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

is stable? What are the corresponding gain and phase margins?

**Solution:** The differentiator circuit is as shown in Fig. 5.1.1. Here  $\tau = RC$

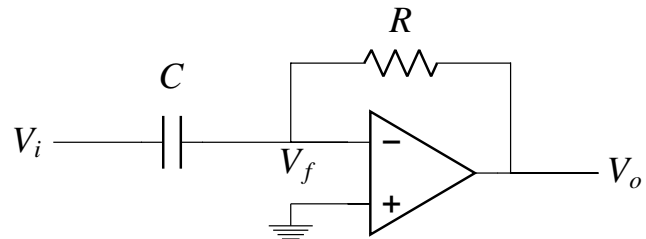


Fig. 5.1.1

For the above circuit using superposition theorem we can write,

$$V_f = \left( \frac{R}{R + \frac{1}{sC}} \right) V_i + \left( \frac{\frac{1}{sC}}{R + \frac{1}{sC}} \right) V_o \quad (5.1.1)$$

5.2. Draw the equivalent control system.

**Solution:**

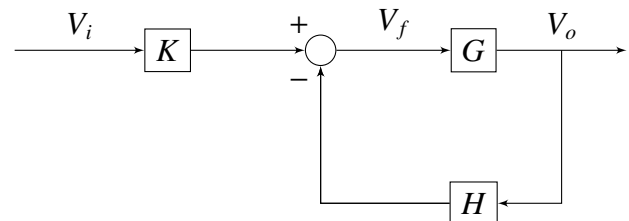


Fig. 5.2

5.3. Find feedback factor H and open loop gain G.

**Solution:** From the above table,

$$H(s) = \frac{1}{1 + sRC} \quad (5.3.1)$$

$$\Rightarrow \frac{1}{H(s)} = 1 + sRC \approx sRC \quad (5.3.2)$$

$$G(s) = \frac{10^3}{\left(1 + \frac{s}{2\pi \cdot 10^6}\right) \left(1 + \frac{s}{2\pi \cdot 10^7}\right)} \quad (5.3.3)$$

5.4. Rate of Closure rule

**Solution:** The rule states that at intersection of

Parameters	Definition	For given circuit
Open loop gain	G	G
Feedback factor	H	$\frac{1}{1+sRC}$
Loop gain	GH	$\frac{G}{1+sRC}$
Gain Factor	K	$\frac{-sRC}{1+sRC}$
Closed loop gain	$K \frac{G}{1+GH}$	$\frac{G(-sRC)}{1+G+sRC}$

TABLE 5.2

$20 \log \left| \frac{1}{H(j\omega)} \right|$  and  $20 \log |G(j\omega)|$  the difference of the slopes (called the rate of closure) should not exceed 20dB/decade.

The Bode plot for  $\frac{1}{|H(j\omega)|}$  has a slope of +20dB/decade. Therefore, the closed-loop amplifier will be stable if  $20 \log \left( \frac{1}{H} \right)$  line intersects the  $20 \log |G|$  curve at a point on the 0dB/decade segment.

The 0dB/decade segment of the  $20 \log |G|$  curve is  $G_o = 10^3$ . We should test the stability at the pole frequency  $\omega_{P1} = 2\pi \cdot 10^6$  which separate the 0dB/decade segment and the -20dB/decade. Thus we can write that as,

$$20 \log |G_o| - 20 \log \left( \frac{1}{H(j\omega_{P1})} \right) \leq 20dB \quad (5.4.1)$$

$$\Rightarrow |G_o H(j\omega_{P1})| \leq 1 \quad (5.4.2)$$

Substituting,

$$G_o \frac{1}{\omega_{P1} \tau} \leq 1 \quad (5.4.3)$$

$$\therefore \tau \geq \frac{G_o}{\omega_{P1}} = \frac{10^3}{2\pi \cdot 10^6} = 159.15\mu s \quad (5.4.4)$$

$$\Rightarrow \tau_{min} = 159.15\mu s \quad (5.4.5)$$

5.5. Find Phase Margin and Gain Margin for  $\tau = \tau_{min}$ .

**Solution:** From the Equation (5.4.5)

$$\text{At, } \tau = \tau_{min} \quad (5.5.1)$$

$$|G_o H(j\omega_{P1})| = 1 \quad (5.5.2)$$

$$\Rightarrow P.M = \angle G(j\omega_{P1}) H(j\omega_{P1}) + 180^\circ \quad (5.5.3)$$

So,

$$\angle G(j\omega_{P1}) = -\tan^{-1} \left( \frac{\omega_{P1}}{2\pi \cdot 10^6} \right) - \tan^{-1} \left( \frac{\omega_{P1}}{2\pi \cdot 10^7} \right) \quad (5.5.4)$$

$$= -50.71^\circ \quad (5.5.5)$$

$$\angle H(j\omega_{P1}) = -90^\circ \quad (5.5.6)$$

$$\Rightarrow P.M = 180^\circ - 50.71^\circ - 90^\circ = 39.29^\circ \quad (5.5.7)$$

$$\therefore P.M = 39.29^\circ \quad (5.5.8)$$

For Gain Margin we need to find  $\omega_{180}$  such that

$$\angle G(j\omega_{180}) H(j\omega_{180}) = -180^\circ \quad (5.5.9)$$

$$\Rightarrow -\tan^{-1} \left( \frac{\omega_{180}}{2\pi \cdot 10^6} \right) - \tan^{-1} \left( \frac{\omega_{180}}{2\pi \cdot 10^7} \right) - 90^\circ = -180^\circ \quad (5.5.10)$$

Solving we get,

$$\omega_{180} = 19.98 \text{ Mrad/s} \quad (5.5.11)$$

The Gain Margin is as follows,

$$GM = -20 \log |G(j\omega_{180}) H(j\omega_{180})| \quad (5.5.12)$$

$$= -20 \log |G(j\omega_{180})| + 20 \log \left| \frac{1}{H(j\omega_{180})} \right| \quad (5.5.13)$$

$$= -49.12 + 70.05 \quad (5.5.14)$$

$$\therefore G.M = 20.93dB \quad (5.5.15)$$